

# Electric Circuits - Homework 04

Automation Class 1904

(Due date: 2020/12/27)

1. (10 Point) Ans:

a).By the question and figure:

right:

$$-2\frac{di_g}{dt} + 16\frac{di_2}{dt} + 32i_2 = 0$$

$$8\frac{di_2}{dt} + 16i_2 = \frac{di_g}{dt}$$

b).From the question :

$$i_2 = e^{-t} - e^{-2t}$$

Then we know:

$$8\frac{di_2}{dt} + 16i_2 = -8e^{-t} + 16e^{-2t} + 16e^{-t} - 16e^{-2t} = 8e^{-t}$$

$$\frac{di_g}{dt} = 8e^{-t}$$

Thus, satisfied.

c).By question b and a:

$$v_1 = 4\frac{di_g}{dt} - 2\frac{di_2}{dt} = 34e^{-t} - 4e^{-2t}$$

d).By the question c:

$$v_1(0) = 30v$$

Yes, it make sense.

2. (10 Points)

a).By the question,  $i_1$  and  $i_2$  is clockwise mesh currents in the left and right.

Then use Mesh-current method:

$$\begin{aligned} v_{ab} &= L_1 \frac{di_1 - i_2}{dt} + M \frac{di_2}{dt} \\ 0 &= L_2 \frac{di_2}{dt} + M \frac{di_1 - i_2}{dt} - L_1 \frac{di_1 - i_2}{dt} - M \frac{di_2}{dt} \end{aligned}$$

Simplified:

$$\begin{aligned} v_{ab} &= L_1 \frac{di_1}{dt} + (M - L_1) \frac{di_2}{dt} \\ 0 &= (L_1 - M) \frac{di_1}{dt} + (L_1 + L_2 - 2M) \frac{di_2}{dt} \end{aligned}$$

Thus:

$$v_{ab} = \left( \frac{L_1 + L_2 - 2M}{L_1 L_2 - M^2} \right) \frac{di_1}{dt}$$

from which we have:

$$L_{ab} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

b).If the magnetic polarity of coil 2 is reversed, the sign of M reverses, therefore

$$L_{ab} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

3. (20 Points)Ans:

With no finger on the button the circuit and  $i = C \frac{dv}{dt}$ , then we know:

$$C_1 \frac{dv-v_s}{i} + C_2 \frac{dv-v_s}{t} = 0$$

$$C_1 = C_2$$

Thus:

$$2C \frac{dv}{dt}$$

With a finger on the button:

$$C_1 \frac{dv-v_s}{i} + C_2 \frac{dv-v_s}{t} + C_3 \frac{dv}{dt} = 0$$

Simplified:

$$(C_1 + C_2 + C_3) \frac{dv}{dt} + C_2 \frac{dv_s}{dt} - C_1 \frac{dv_s}{dt} = 0$$

$$C_1 = C_2 = C_3$$

Thus:

$$3C \frac{dv}{dt} = 0$$

Since, there is no change in the output voltage of this circuit.

4. (10 Points)

Ans:  $t < 0$ :

$$i_L = \frac{2.5v_0}{v_0} = 2.5A$$

$t > 0$ : Find Thevenin resistance seen by inductor:

$$i_T = 2.5A$$

$$R_{Th} = \frac{v_T}{i_T} = 0.4$$

Thus:

$$\tau = \frac{L}{R} = 12.5ms$$

$$\frac{1}{\tau} = 80$$

Then:

$$i_0 = 2.5e^{-80t}A$$

$$v_0 = L \frac{di_0}{dt} = -e^{-80t} \quad t \geq 0$$

5. (10 Points)

Ans:

a).By the question and figure

$$v_0(0^-) = v_0(0^+) = 120V$$

Make  $2.5k\Omega$  resistor the right hand to Source Transformation.we will get resistor  $37.5k\Omega$  and source  $150V$  series.

$$v_0 = -150V$$

$$R_{eq} = 50k\Omega$$

then:

$$\tau = RC = 1.6ms$$

$$\frac{1}{\tau} = 625$$

Thus:

$$v_0 = -150 + (120 - (-150))e^{-625t}$$

$$v_0 = -150 + 270e^{-625t}$$

b).By the question:

$$i_0 = C \frac{dv}{dt} = 6.75e^{-625t}mA$$

c).By the question:

$$v_g = v_0 - 2.5 \times 10^3 = -150 + 253.125e^{-625t}$$

d).By the question c:

$$v_g(0) = 103.125V$$

6. (10 Points)

Ans:

When  $0 \leq t \leq 200\mu s$ :

$$R_{eq} = 150 || 100 = 60k\Omega$$

$$\tau = RC = 200\mu s$$

$$\frac{1}{\tau} = 5000$$

Thus:

$$v_c = 300e^{-5000t}$$

$$v_c(200\mu s) = 110.36$$

when  $200\mu s \leq t \leq \infty$ :

$$R_{eq} = 30 || 60 + 120 || 40 = 50K\Omega$$

$$\tau = R_{eq}C = 166.67\mu s$$

$$\frac{1}{\tau} = 6000$$

Thus:

$$v_c = 110.36e^{-6000(t-200\mu s)}V$$

When  $t = 300\mu s$ :

$$v_c(300\mu s) = 110.36e^{-6000(100\mu s)} = 60.57V$$

$$i_0(300\mu s) = \frac{v_c}{R_{eq}} = 1.21mA$$

Then:

$$i_1 = \frac{60}{90}i_0 = \frac{2}{3}i_0 = 0.8067mA(\text{direction down});$$

$$i_2 = \frac{40}{160}i_0 = \frac{1}{4}i_0 = 0.3025mA(\text{direction down});$$

$$i_{mid} = i_1 - i_2 = \frac{5}{12}i_0 = 0.5mA(\text{direction right})$$

7. (20 Points)

Ans:

By the question and figure: Find Thevenin resistance seen by capacitor

$$v_T = 13 \times 10^4 i_\Delta + (20k\Omega || 80k\Omega) i_T$$

$$i_\Delta = -\frac{20}{100} i_T = -0.2 i_T$$

Then:

$$v_T = -10 \times 10^3 i_T$$

Thus:

$$R_{Th} = \frac{v_T}{i_T} = -10k\Omega$$

$$\tau = R_{Th}C = -0.025$$

$$\frac{1}{\tau} = -40$$

Since:

$$v_c = 20e^{40t}V$$

when  $v_c = 20000V$

$$40t = \ln 1000$$

$$t = 172.69ms$$

8. (10 Points)

Ans:

a).By the question and figure, When  $0 \leq t \leq 0.5$ :

$$i = \frac{21}{60} + \left(\frac{30}{60} - \frac{21}{60}\right)e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{R}$$

Thus :

$$i = 0.35 + 0.15e^{-\frac{60t}{L}}$$

When  $t = 0.5$ :

$$i(0.5) = 0.35 + 0.15e^{-\frac{30}{L}} = 0.40$$

So:

$$e^{-\frac{30}{L}} = 3;$$

$$L = \frac{30}{\ln 3} = 27.31H$$

b).Hypothesized  $t_r$  is the time the relay releases:  $0 \leq t \leq t_r$

$$i = 0 + \left(\frac{30}{60} - 0\right)e^{-\frac{60t}{L}} = 0.5e^{-\frac{60t}{L}}$$

When  $i = 0.4$ , the relay released:

$$0.4 = 0.5e^{-\frac{60t_r}{L}}$$

Thus:

$$t_r = \frac{27.31 \ln 1.25}{60} \cong 0.1s$$