


Electric Circuits - Homework 03

Automation Class 1904


(Due date: 2020/10/5)

1. (10 Point)

Ans:

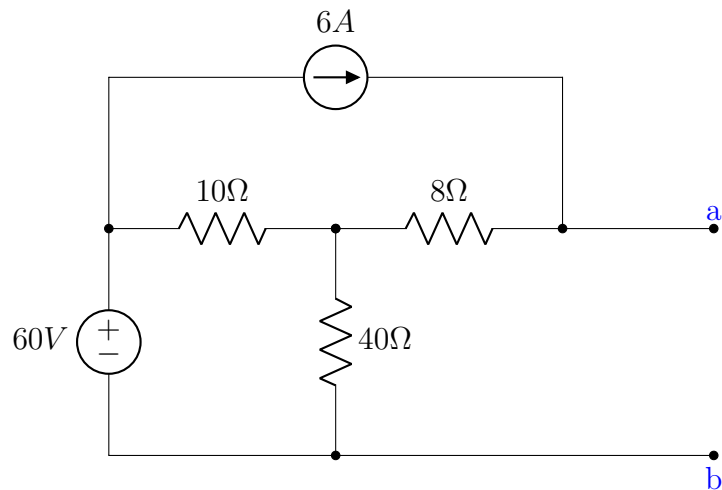

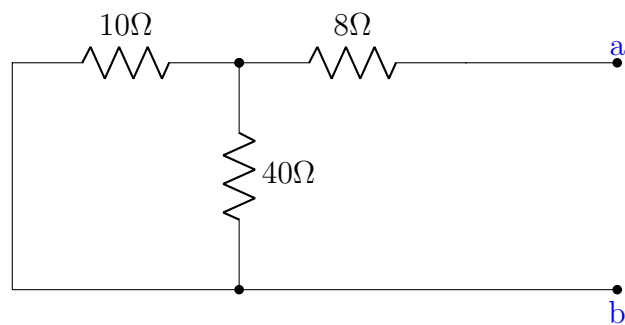
We make the voltage source and the current source deactivated.



Then we can calculate the equivalent resistance R_{eq} ;

$$R_{eq} = 8 + 10 || 40 = 16\Omega$$

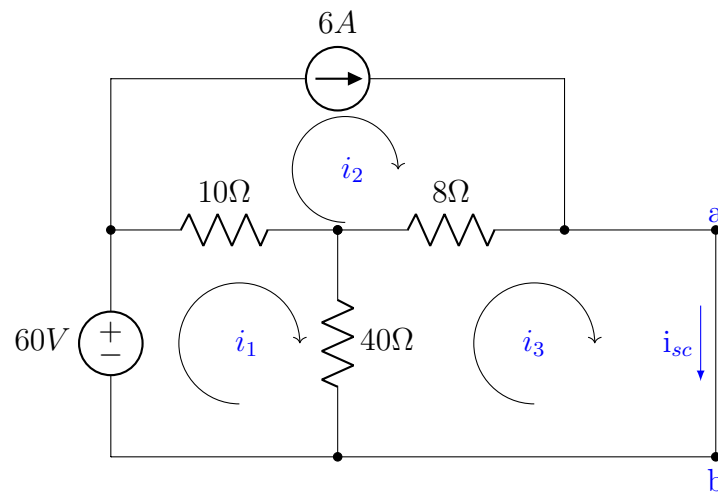The next step is to replace a short circuit across the terminals:



and use the Mesh-Current method calculate the resulting short-circuit current:

$$10(i_1 - i_2) + 40(i_1 - i_3) - 60 = 0$$

$$10(i_2 - i_1) + 8(i_2 - i_3) = 0$$

$$8(i_3 - i_2) + 40(i_3 - i_2) = 0$$


$$i_2 = 6A$$

$$i_3 = i_{sc}$$

Thus the i_{sc} is equal:


$$i_{sc} = 5.25A$$

The circuit shown in:

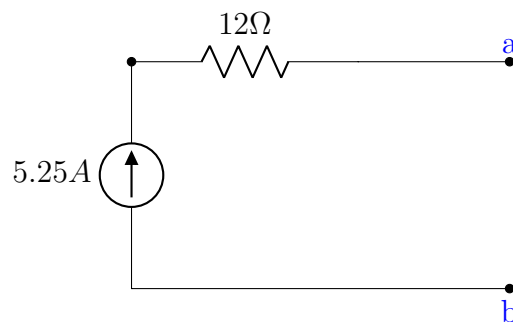

2. (10 Points)

Ans:

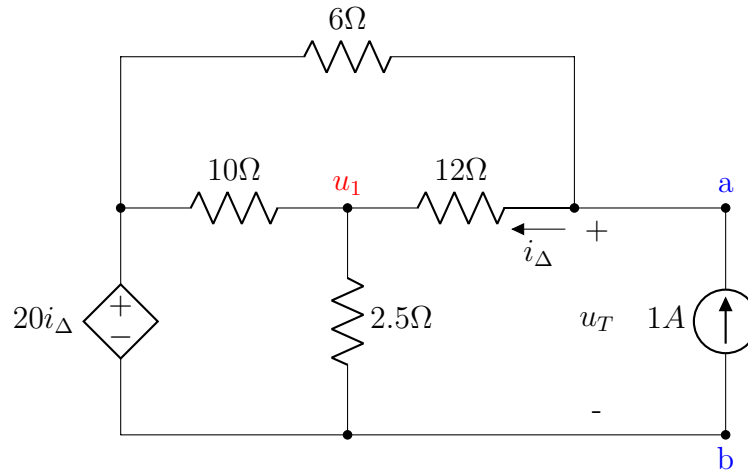

Because there no independent source, so $v_{Th} = 0$; Add a independent current source for 1A at port ab;

According the Node-Voltage method:

$$\begin{aligned}\frac{u_1 - 20i_\Delta}{10} + \frac{u_1 - u_T}{12} + \frac{u_1}{2.5} &= 0 \\ \frac{u_T - 20i_\Delta}{6} + \frac{u_T - u_1}{12} - 1 &= 0 \\ \frac{u_T - u_1}{12} &= i_\Delta\end{aligned}$$

We can get :

$$i_\Delta = 1.5A \quad u_1 = 9V \quad u_T = 27V$$

if we add a independent current course for 2A at port ab:


$$i_\Delta = 3A \quad u_1 = 18V \quad u_T = 54V$$

Thus when we add a independent current course for nA at port ab:


$$i_\Delta = 1.5nA \quad u_1 = 9nV \quad u_T = 27nV$$

3. (20 Points)

Ans:

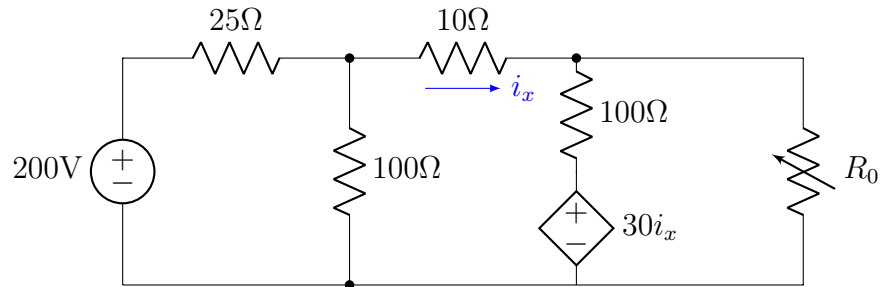

Using Source Transformation to be:

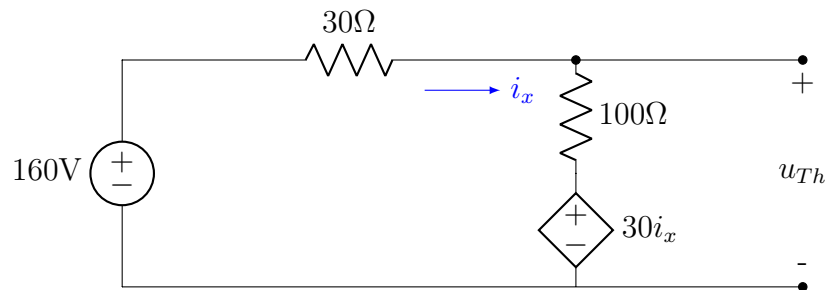

then we can calculate i_x :


$$\frac{160 - 30i_x}{130} = i_x$$

$$i_x = 1A$$

since

$$u_{Th} = 100i_x + 30i_x = 130V$$

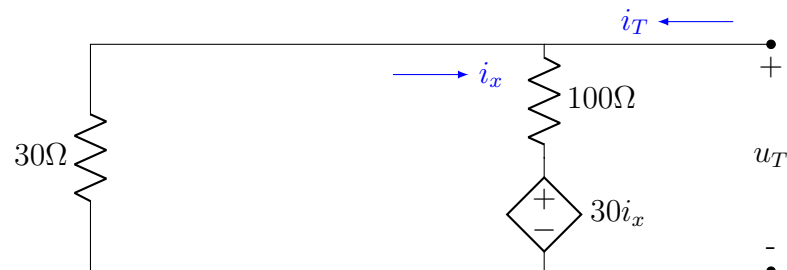Using the test-source method to find the Th'evenin resistance gives:



Thus use KCL:

$$i_x = -u_T/30$$

$$i_T = -i_x + \frac{u_T - 30i_x}{100}$$

$$R_{eq} = \frac{u_T}{i_T} = 18.75\Omega$$

Then :


$$P = i^2 \times R = \left(\frac{u_{Th}}{R_{eq} + R_0}\right)^2 \times R_0 = 225W$$

Thus :


$$R_0 = \frac{625}{36}\Omega \quad R_0 = \frac{81}{4}\Omega$$

4. (10 Points)

Ans:

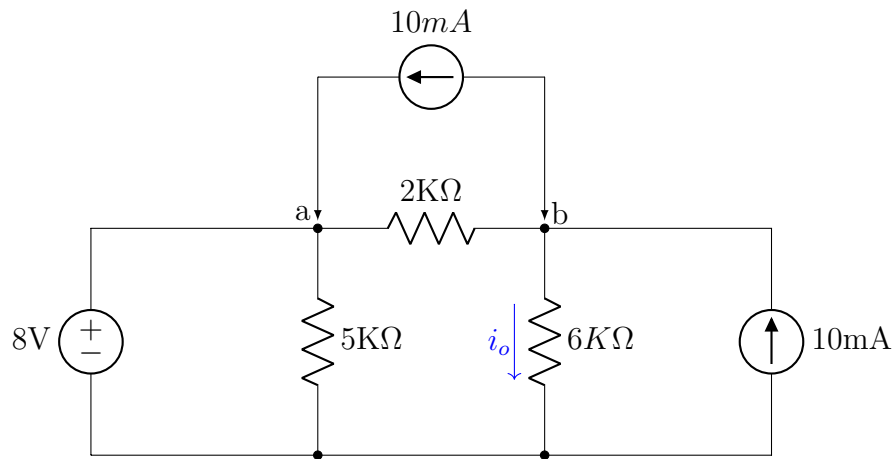

By hypothesis $i'_o + i''_o = i_o$:

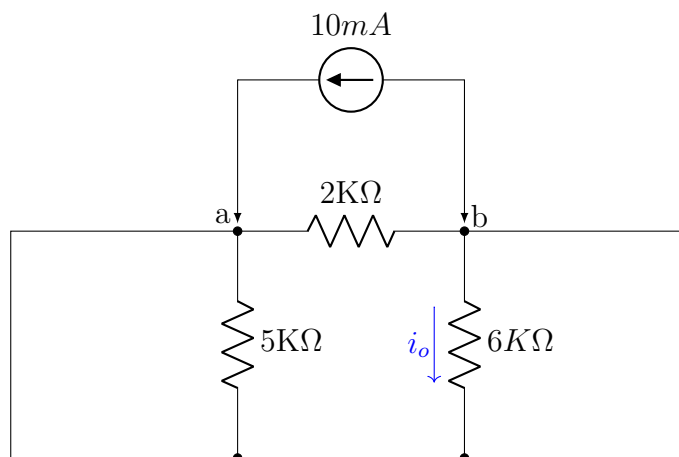

$$i''_o = 10 \times \frac{2}{2+6} = 2.5mA$$

$$i'_o = i_o - i''_o = 1mA$$


Using KCL to find the value of i_o after the current source is attached:

$$\frac{U'_b - 8}{2000} + \frac{U'_b}{6000} + 0.01 - 0.01 = 0$$

$$u'_b = 6V \quad i'_o = U_b/6000 = 1mA$$

5. (10 Points)

Ans:

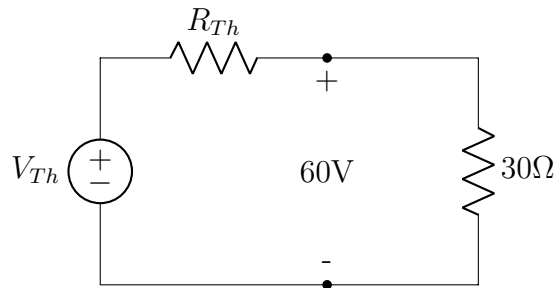

According to the question :

$$V_{Th} = 75V \quad i = \frac{v_0}{R_L} = \frac{60}{30} = 2A$$

Thus :

$$R_{Th} = \frac{75-60}{2} = 7.5\Omega$$

and:

$$\frac{V_{Th}}{R_{Th} + R_L} = \frac{v_0}{R_L}$$

Since:

$$R_{Th} = \left(\frac{V_{Th}}{v_0} - 1 \right) R_L$$

6. (10 Points)

Ans:

a). We known from the question:

$$t : 0 \rightarrow 250\mu s \quad (250 \times 10^{-6}s) \quad C : 0.2\mu F \quad (0.2 \times 10^{-6}F)$$

$$v_0 : -100V \quad i : 100e^{-1000t}mA \quad (0.1e^{-1000t}A)$$

because of :

$$i = C \frac{dV}{dt};$$

Thus:

$$v = \frac{1}{0.2 \times 10^{-6}} \int_0^{250 \times 10^{-6}} 0.1 e^{-1000t} dt - 100$$

Then we can calculate V:

$$v = 500(1 - e^{-0.25}) - 100 = 10.6V$$

because of:

$$w = \frac{1}{2} C v^2$$

Thus :

$$w = 0.5 \times 0.2 \times 10^{-6} \times 10.6^2 = 1.1236 \times 10^{-5} J = 11.236 \mu J$$

b). Because of $t \rightarrow \infty$;

Thus :


$$u_{\infty} = 500 - 100 = 400V$$

Since :


$$w_{\infty} = 0.5 \times 0.2 \times 10^{-6} \times 400^2 = 0.016 J = 1.6 \times 10^4 \mu J$$

7. (20 Points)

Ans:

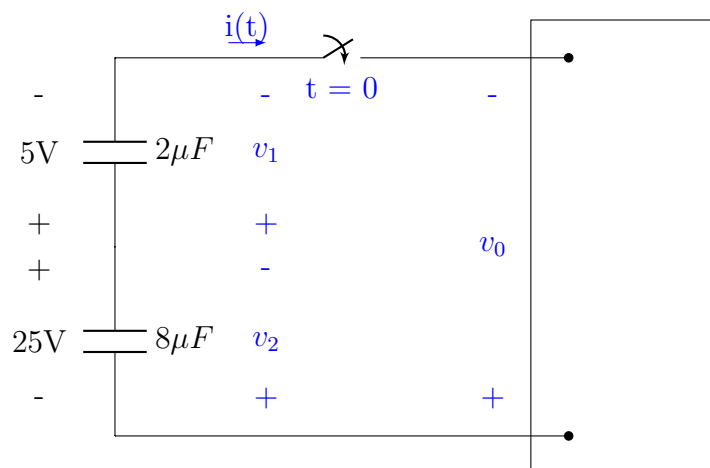

a).

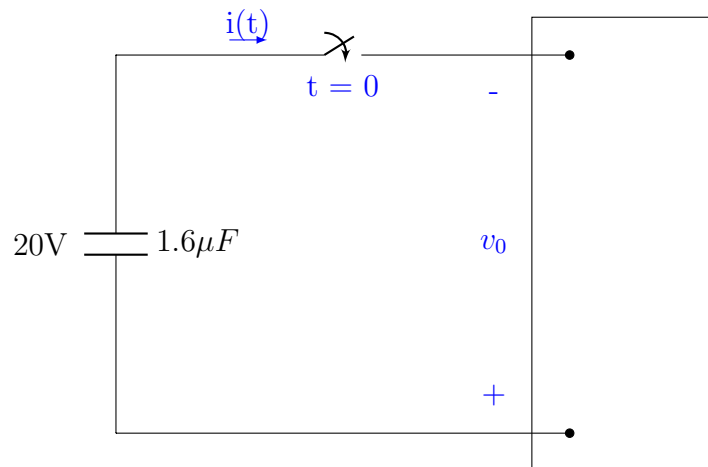

Because of :

$$i = C \frac{dV}{dt};$$

Thus:

$$v_0 = \frac{1}{1.6 \times 10^{-6}} \int_0^t 960 \times 10^{-6} e^{-30t} dt - 20$$

$$v_0 = -20e^{-30t} V, \quad t \geq 0$$

b). In a similar way:

$$v_1 = \frac{1}{2 \times 10^{-6}} \int_0^t 960 \times 10^{-6} e^{-30t} dt + 5$$

$$v_1 = -16e^{-30t} + 21(V), \quad t \geq 0$$

c). In a similar way:

$$v_2 = \frac{1}{8 \times 10^{-6}} \int_0^t 960 \times 10^{-6} e^{-30t} dt - 25$$

$$v_2 = -4e^{-30t} - 21(V), \quad t \geq 0$$

d). From a). we known v_0 , then we can calculate p and w :

$$p = -vi = -(-20e^{-30t})(960 \times 10^{-6} e^{-30t}) = 1.92 \times 10^{-2} e^{-60t}$$

$$w_{\infty} = \int_0^{\infty} 1.92 \times 10^{-2} e^{-60t} dt = 3.2 \times 10^{-4} J = 320 \mu J$$

e). Because of $w = \frac{1}{2} C v^2$

$$w = 0.5 \times (2 \times 10^{-6}) \times 5^2 + 0.5 \times (8 \times 10^{-6}) \times 25^2 = 2525 \mu J$$

f).


$$w_{trapped} = w_{initial} - w_{delivered} = 2525 - 320 = 2205 \mu J$$

g). When $t \rightarrow \infty$:

$$v_1 = 21V \quad v_2 = -21V$$

$$w = 0.5 \times (2 \times 10^{-6}) \times 21^2 + 0.5 \times (8 \times 10^{-6}) \times (-21)^2 = 2205 \mu J$$

Ans:

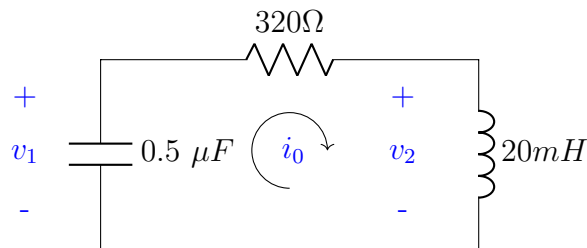

From the question :

$$i_0 = 50e^{-8000t}(\cos 6000t + 2\sin 6000t) mA = 0.05e^{-8000t}(\cos 6000t + 2\sin 6000t) A$$

Then we can calculate:

$$\frac{di_0}{dt} = e^{-8000t}(200\cos 6000t - 1100\sin 6000t)$$

$$\frac{di_0}{dt}(0^+) = 1 \times (200 - 0) = 200$$

So $v_2(0^+) = L \frac{di_0}{dt}(0^+)$:

$$v_2(0^+) = 20 \times 10^{-3} \frac{di_0}{dt}(0^+) = 4V$$

And $v_C = v_R + v_L$:

$$i_0(0^+) = 0.05A$$

$$v_1(0^+) = 320i_0(0^+) + v_2(0^+) = 20V$$